
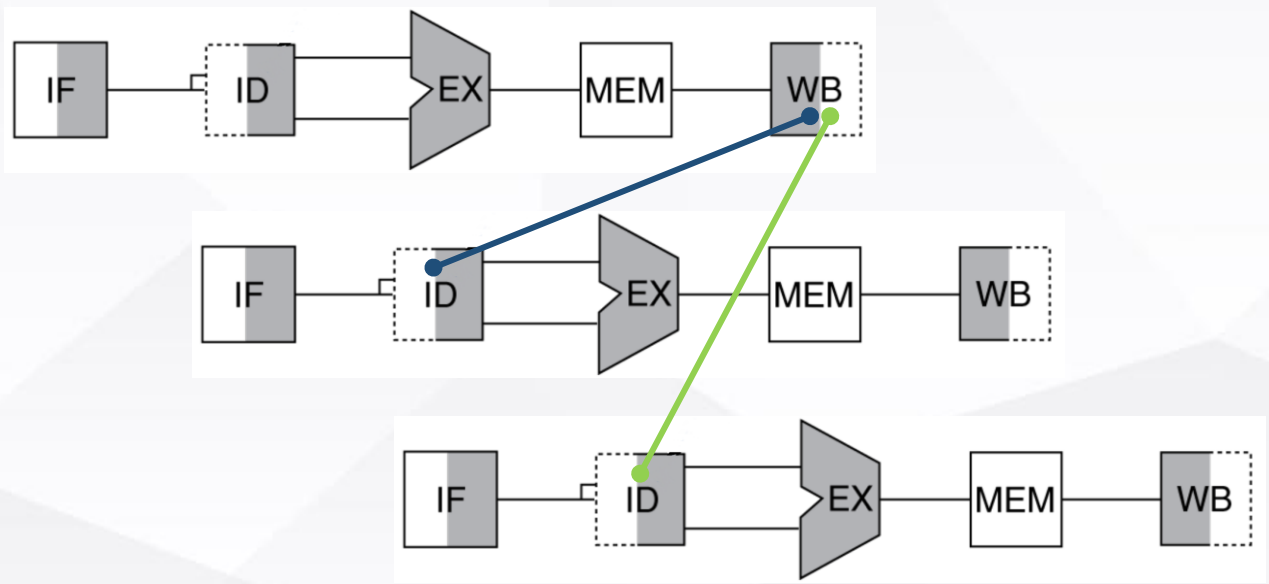


ECE3700J Mid RC Data Hazard

Presenter: Ruan Renjian 阮仁剑

Data Hazard in ALU Instructions

Time (in clock cycles)									
Value of register x2:	CC 1	CC 2	CC 3	CC 4	CC 5	CC 6	CC 7	CC 8	CC 9
	10	10	10	10	10/-20	-20	-20	-20	-20

 


Solution with adding NOP/Stall


```

nop    # no operation, pseudo-instruction
        # addi x0, x0, 0
  
```

EX Hazard: +2 NOP

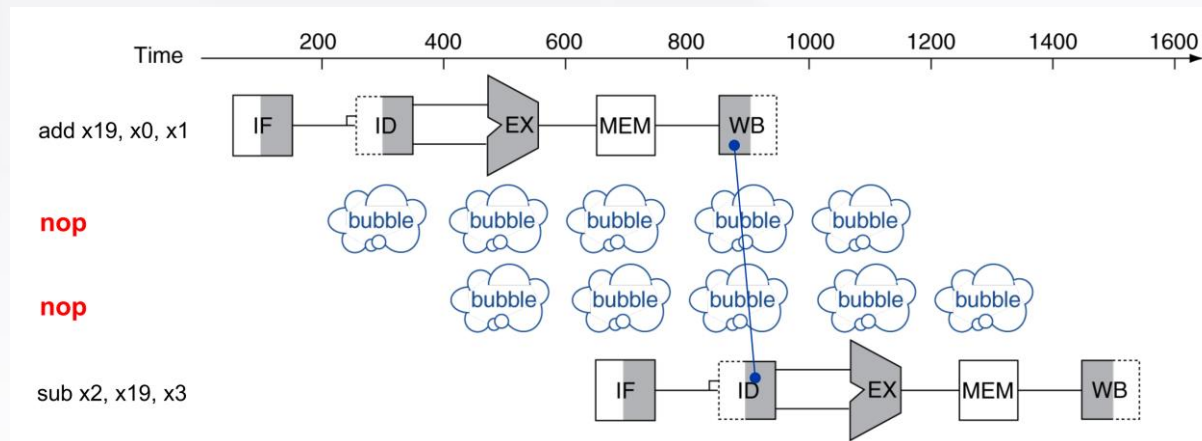

MEM Hazard: +1 NOP

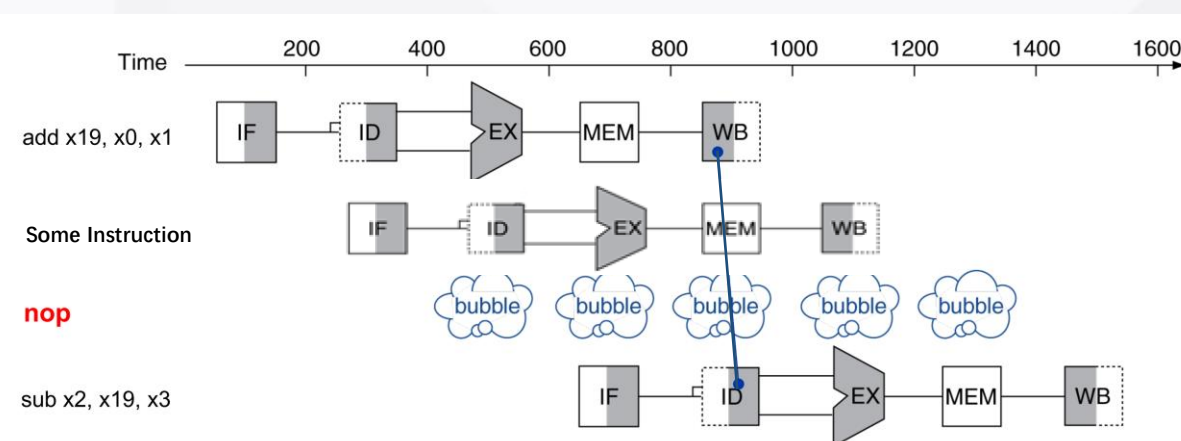

Solution with forwarding

Forwarding Scheme

Time (in clock cycles)	CC 1	CC 2	CC 3	CC 4	CC 5	CC 6	CC 7	CC 8	CC 9
Value of register x2:	10	10	10	10	10/-20	-20	-20	-20	-20

Program execution order (in instructions)

sub x2, x1, x3
and x12, x2, x5
or x13, x6, x2


Forwarding

EX hazard

MEM hazard

Forwarding Paths


Forwarding Unit in EX stage

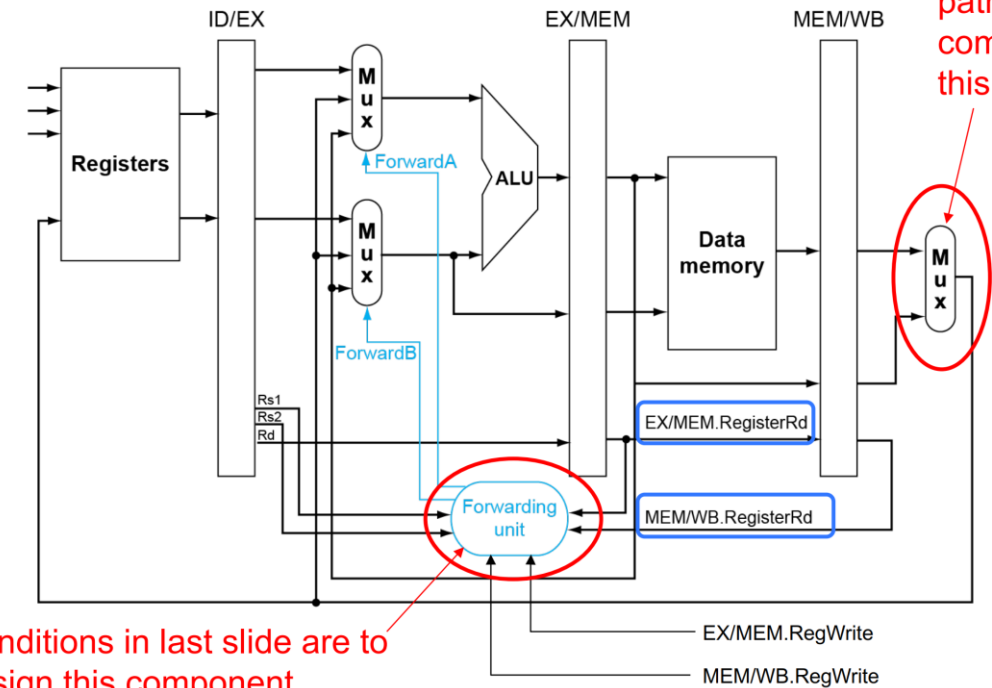

Conditions in last slide are to design this component

Solution with forwarding


Forwarding detection and MUXes

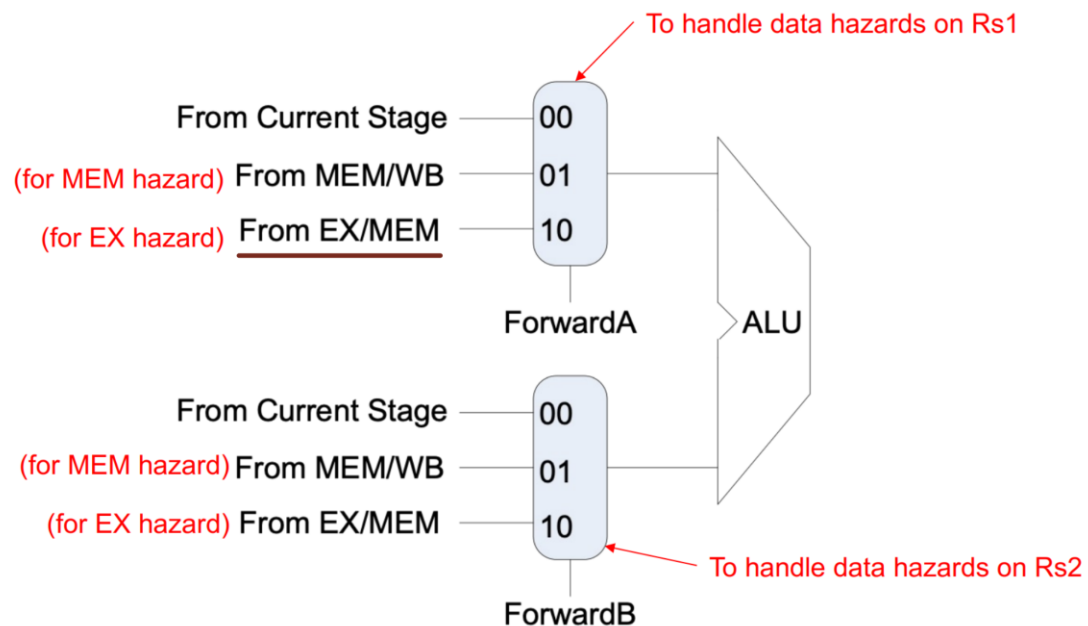


```

if (EX/MEM.RegWrite && (EX/MEM.RegisterRd ≠ 0) && (EX/MEM.RegisterRd ==
ID/EX.RegisterRs1)) // EX hazard
    ForwardA = 10
else if (MEM/WB.RegWrite && (MEM/WB.RegisterRd ≠ 0) && (MEM/WB.RegisterRd =
ID/EX.RegisterRs1) // MEM hazard
    ForwardA = 01
if (EX/MEM.RegWrite && (EX/MEM.RegisterRd ≠ 0) && (EX/MEM.RegisterRd ==
ID/EX.RegisterRs2)) // EX hazard
    ForwardB = 10
else if (MEM/WB.RegWrite && (MEM/WB.RegisterRd ≠ 0) && (MEM/WB.RegisterRd =
ID/EX.RegisterRs2) // MEM hazard
    ForwardB = 01;
  
```

Load-use Data Hazard

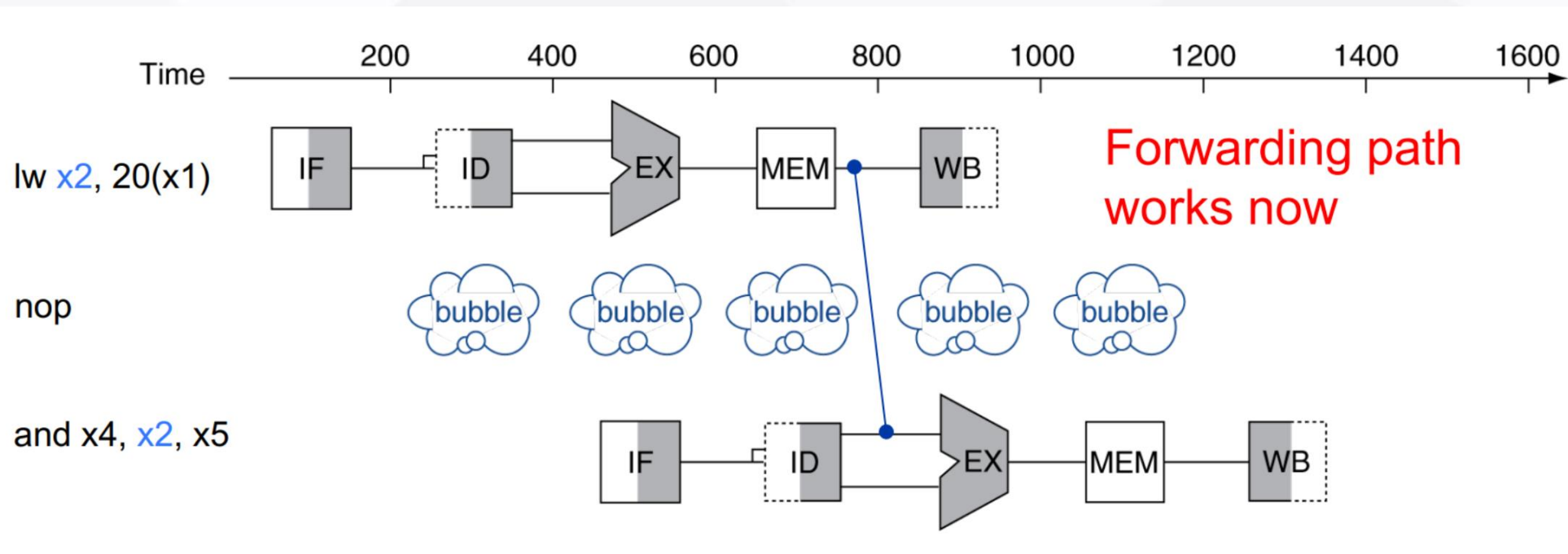

Load-use Data Hazard

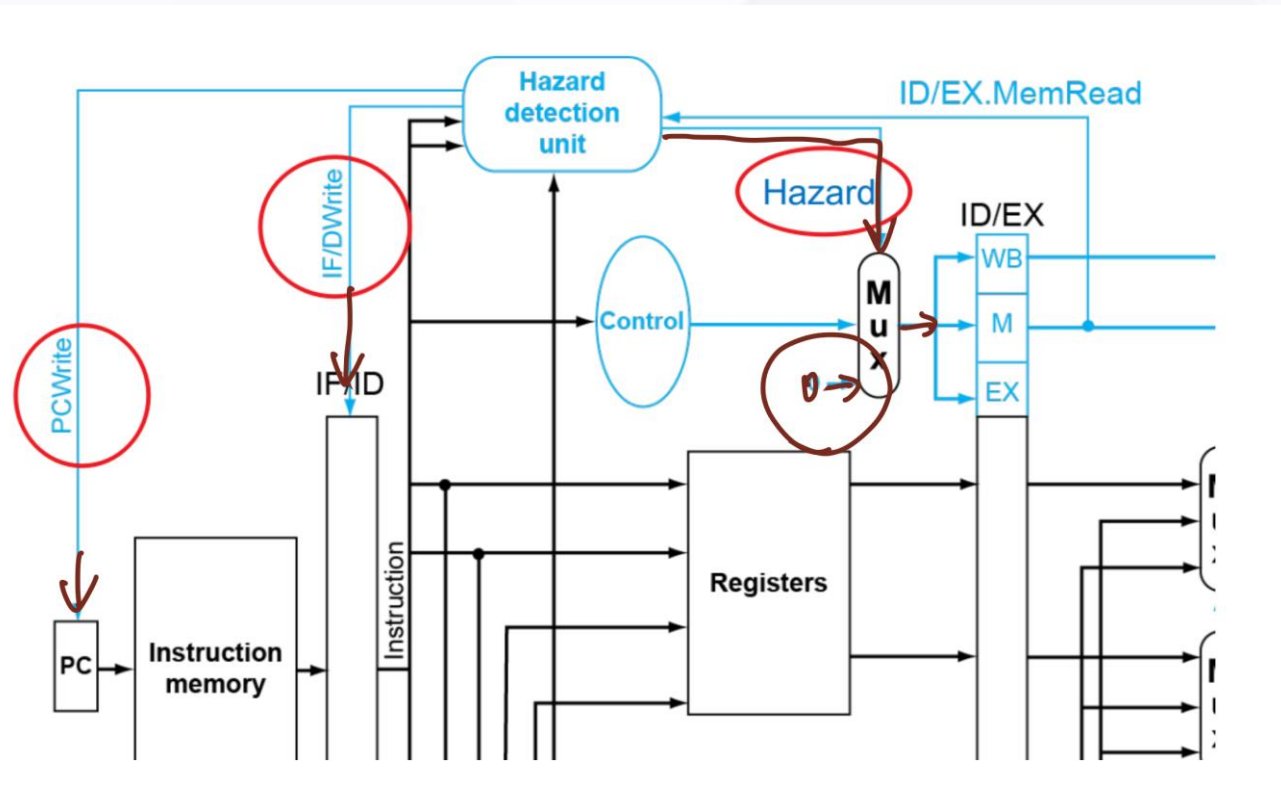

```

if (ID/EX.MemRead && (ID/EX.rd == IF/ID.rs1 || ID/EX.rd == IF/ID.rs2)) {
  PCWrite = 0;
  IF/IDWrite = 0;
  Hazard = 1;
}
else {
  PCWrite = 1;
  IF/IDWrite = 1;
  Hazard = 0;
}
  
```


Very Important !!! (Slide 31-37)

CC1

PC Write	IF/ID Write	Hazard	ID/EX. MemRead	IF/ID. Rs1	IF/ID. Rs2	ID/EX. Rd
1	1	x	x	x	x	x

lw x2, 20(x1)

CC2

PC Write	IF/ID Write	Hazard	ID/EX. MemRead	IF/ID. Rs1	IF/ID. Rs2	ID/EX. Rd
1	1	x	x	1	20	x

and x4,x2,x5 lw x2, 20(x1)

CC3

PC Write	IF/ID Write	Hazard	ID/EX. MemRead	IF/ID. Rs1	IF/ID. Rs2	ID/EX. Rd
0	0	1	1	2	5	2

or x8,x2,x6 and x4,x2,x5 lw x2, 20(x1)

CC4

PC Write	IF/ID Write	Hazard	ID/EX. MemRead	IF/ID. Rs1	IF/ID. Rs2
1	1	0	0	2	5

or x8,x2,x6 and x4,x2,x5 nop (and) lw x2, 20(x1)

CC4

ID/EX.Rs1	ID/EX.Rs2	ID/EX.Rd	EX/MEM.Rd	MEM/WB.Rd
2	5	4	2	x
EX/MEM.RegWrite	MEM/WB.RegWrite	ForwardA	ForwardB	
1	x	10	00	



CC5

PC Write	IF/ID Write	Hazard	EX/MEM. MemRead	EX/MEM. MemWrite	
1	1	0	0	0	No effective operation

add x9,x4,x2 or x8,x2,x6 and x4,x2,x5 nop (and) lw x2, 20(x1)

CC5

ID/EX.Rs1	ID/EX.Rs2	ID/EX.Rd	EX/MEM.Rd	MEM/WB.Rd
2	5	4	4	2
EX/MEM.RegWrite	MEM/WB.RegWrite	ForwardA	ForwardB	
0	1	01	00	



TIPS

- Slide and homework are VERY Important!
- Understand how processor functions at different stages
(Your Vivado Labs can help you well)
- Be careful

Thank You and Good Luck :D